

ALL CMOS Logic Circuits  
can be divided into  
TWO PARTS:

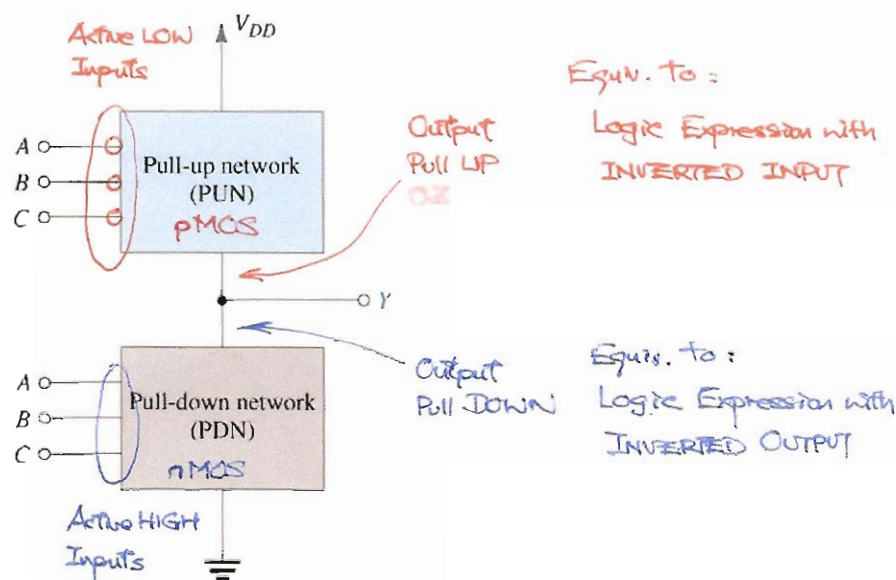


Figure 10.8 Representation of a three-input CMOS logic gate. The PUN comprises PMOS transistors, and the PDN comprises NMOS transistors.



 


Figure 10.11 Usual and alternative circuit symbols for MOSFETs.

 
AND  $\Leftrightarrow$  Serial Connection



$$Y = \bar{A} \cdot \bar{B}$$

 

$$\bar{Y} = A + B$$

 

OR  $\Leftrightarrow$  Parallel Connection

Figure 10.12 A two-input CMOS NOR gate.

 


Figure 10.13 A two-input CMOS NAND gate.

Example = nMOS Pull-Down Networks

 


Figure 10.9 Examples of pull-down networks.

Example: pMOS Pull-Up Networks

 


Figure 10.10 Examples of pull-up networks.