

Electric Circuit ㄉㄉ學

9/18

blahblahblah:

- cloud computing
- multicore (parallel programming)
- embedded software
- consumer application mobile apps


in our course:

- electric circuits
- 電子元件
- basic electric circuit
- 60% are concepts

Grading:


- 3-4 homeworks
- midterm
- final

Textbook: Microelectronic Circuits 6/e

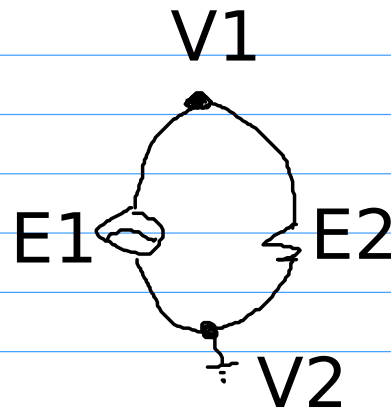

electric circuits

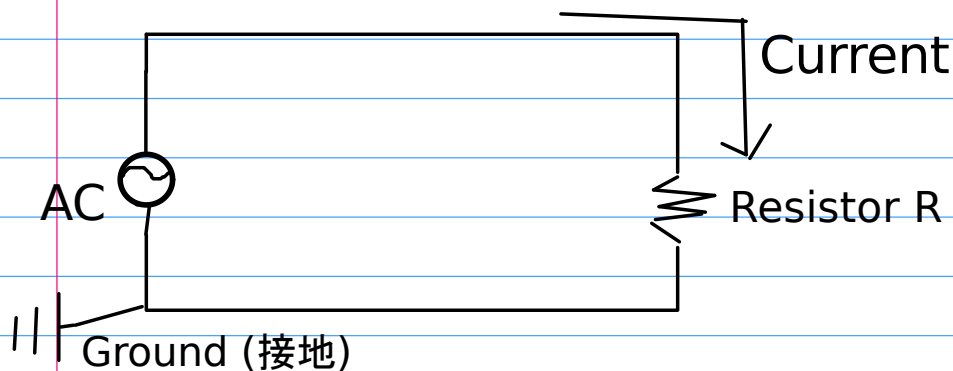- components / devices # 元件
- graph
 - vertices (distinct electric potential) # compare to ground $V=0$
 - edges (components)
- to represent the connections between electric components
- must be at least one component (or more) between vertices
- Edge 必對稱於 component
- voltage
 - the difference between two vertices



9/20

basic electrical circuit theory

basic concept:

- circuit
- voltage / current / power
- signal
 - AC/DC
 - RMS

Definition of electric circuits:

- a graph, connections of vertices and edges, whereby every edge contains exact one electric component (Active | Passive*).

And every vertex has a specific electric potent, where one of them is defined as 0 volt, i.e. ground

* active (generating power), passive (consuming power)

measurement:

- electric potential # for vertex
- current # for edge
- electric power
- V.I.P. !

$$\varepsilon = 1/2 mv^2$$

$$\rho = mv$$

能量守恒 Hamiltonian

動量守恒 Newtonian

Ohm's Law:


- $V = IR$
- R's definition $\Rightarrow V / I$

$$R = \rho L / A = V / I$$

$$E = V / L = \rho I / A \quad \# \text{ 電場, electric field strength}$$

$$J = I / A \quad \# \text{ current density}$$

$$E = \rho J$$

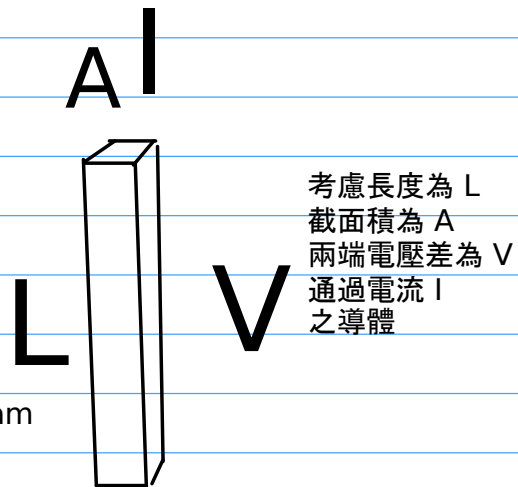


9/25

Basic electric circuits

- basic circuits concept
 - signal
 - devices
 - passive : RHL
- KVL / KCL Kirchhoff's Voltage & Current Law
 - theoretical formulation
 - pragmatic solution
- Equivalent Circuits (等效線路)
 - Thevenin Equiv. (voltage based)
 - Norton's Equiv. (current based)
 - [duality]
- independent concepts
 - generalized concepts of resistance

two port circuits

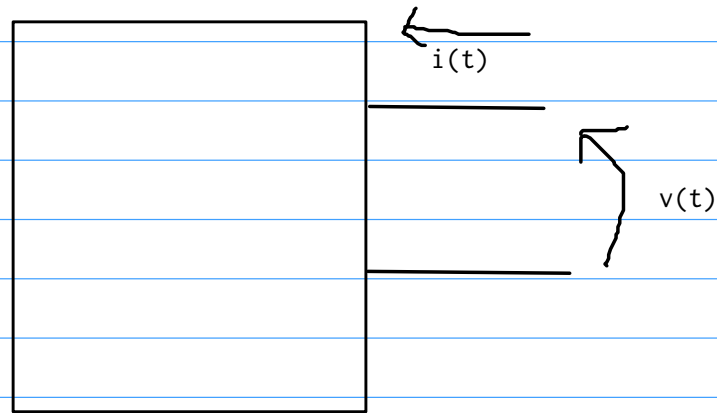

$$Z = V / I$$

一般化的電路：


input impedance => transfer function => output impedance # 線性代數 (?)

LTI system, Linear time-invariant system

=> observation window 要先定好

circuit cascade (串聯)

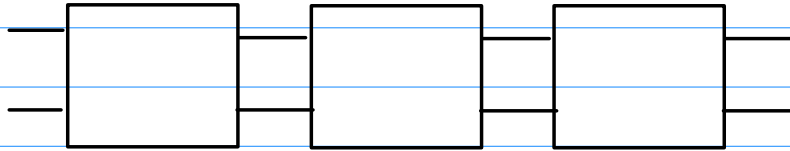- to find the best matching (coupling, 耦合)



time domain analysis

- signal as waveform (波形)

Frequency domain analysis

- signal as a spectra (譜)
- system frequency response
=> Laplace & Fourier transforms

voltage source => signal source

Ohm's Law

邵: 這個大家都知道, 一點都不好玩 QQ

$$i(t) = v(t) / R$$

notation:

- when v, i in lower case => time varying
AC value (X)

V_A => reference to ground


V_a => V_A average

DC value

$$V_s(t) = V_A(t)$$

$$V_A(t_0) \Rightarrow V_A(t) \text{ at } t_0$$
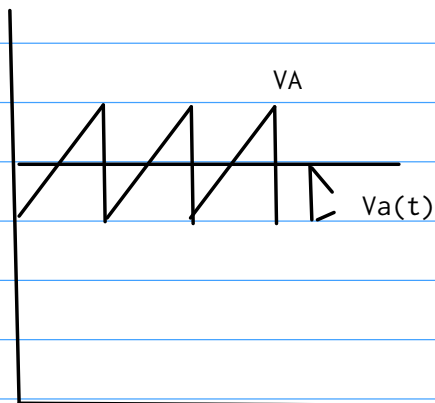
$$V_a(t) = V_A(t) - V_A \Rightarrow \text{AC value (0)}$$



Graph in Electric Circuits

- Every vertex has a distinct voltage
- Every edge has a distinct current

$i_R(t) \Rightarrow$ Edge, component actual value = compare to zero current

$I_R \Rightarrow$ Average of i_R DC value constant

$i_r(t) \Rightarrow$ AC value = $i_R(t) - I_R$

RMS

Richard Matthew Stallman (X)

Rooted Mean Squared

$$V_a = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} v_{\tau}^2(\tau) d\tau} \quad \Leftrightarrow \quad \sqrt{\frac{1}{3}(a^2 + b^2 + c^2)}$$

$P = IV$

Electric power = current * Voltage

$$P_{\tau}(t) = \frac{1}{T} \int_{t_0}^{t_0+T} i(\tau) v(\tau) d\tau$$

$$\text{Apply Ohm's Law : } i_R(t) = \frac{V_A(t)}{R}$$

$$P_{\tau}(t) = \frac{1}{T} \int_{t_0}^{t_0+T} \frac{v_A^2(t)}{R} d\tau$$

$$\propto \frac{1}{T} \int_{t_0}^{t_0+T} v_A^2(t) d\tau$$

$$\propto (v_A^{rms})^2$$

$$P_{\tau}(t) = \frac{(v_A^{rms})^2}{R}$$

9/27

Basic electric component


- Active
 - voltage / current sources
 - independent / dependent
- Passive
 - resistors
 - capacitors (電容)
 - Inductors (電感)
- Linearly and time invariance
- abstract models, maybe not real
- only to show some characteristics of components

Active components

- producer / generator of 'signal' power
- energy transfer => AC -> DC -> waveform
- waveform generator

$V_I(t)$: voltage input
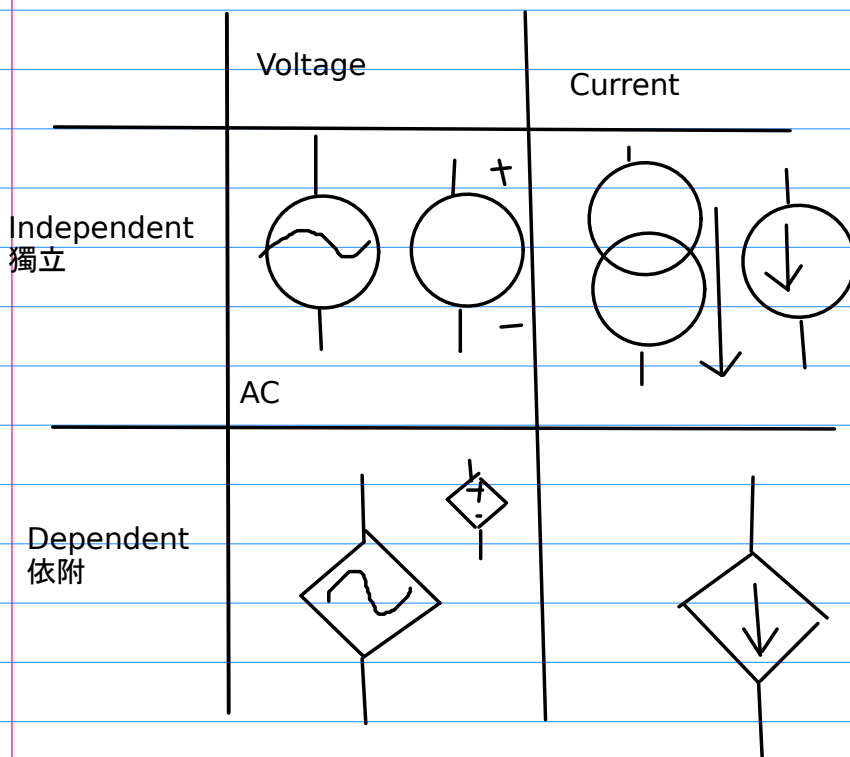
$$P_I(t) = \frac{1}{RT} \int_{t_0}^{t_0+T} v_I^2(\tau) d\tau$$





independent:

- Signal characteristics / amplitude / frequency / phase not dependent on other electric measurements in the circuits

dependent:

- Signal characteristics / amplitude / frequency / phase dependent on other electric measurements in the circuits


Bipole Junction Transistor(BJT)

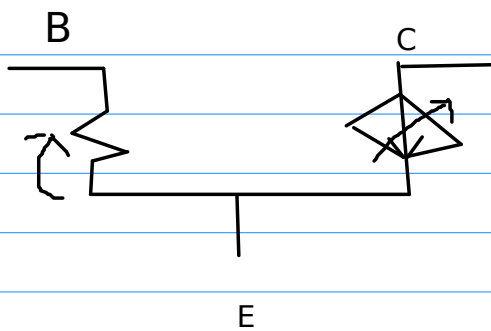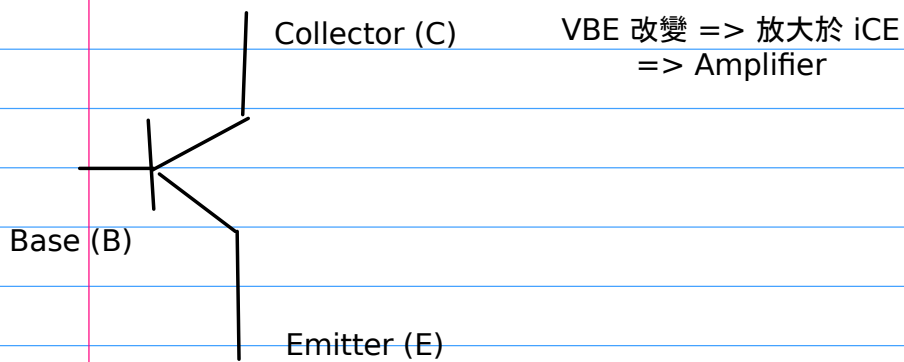

$$i_{CD} = g_m V_{BE}$$

$$g_m = \frac{i_{CE}}{V_{BE}}$$

$$= \frac{i_{input}}{V_{input}}$$

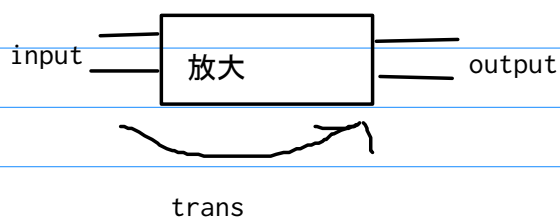

trans-conductance 電導量
gain (增益)

Passive components

- consume signal power
- resistor / capacitor / inductor
- => linear components

linear system

a system 滿足 law of superposition (疊加)

$$ax_1(t) + bx_2(t) \Rightarrow ay_1(t) + by_2(t)$$

$$S(ax_1 + bx_2) \Rightarrow aS(x_1) + bS(x_2)$$

time invariance

邵：我現在嚇你一跳，五秒鐘後我再嚇你一跳，你就不怕了嘛~

10/2

Basic concepts

- electric components
 - passive components (idealized)
 - Resistor (R)
 - Capacitor (C)
 - Inductor (I)

Resistor

碳模電阻 => 紋理愈細 => L 愈大 R 愈大




v-i characteristic (電器特別)

Ohm's Law

$$V = IR$$

v-i char diagram


Line 理想上是直線
斜率是電阻
理想是常數

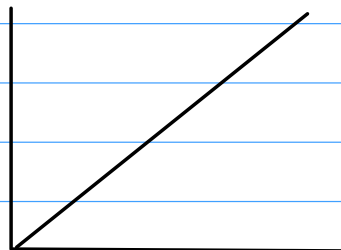

Thermal effect (熱效應)


- produce heat when operating
- 溫度上升 電阻率係數 電阻下降
- 對於良好的導體而言，電子運動近似於 ideal gas
- Thermal run away => 愈來愈熱 => 功率上升 => 燒掉囉 ^q^

Capacitor

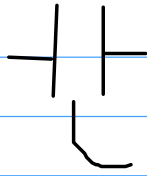

insulator (絕緣體) medium 或是 Air medium

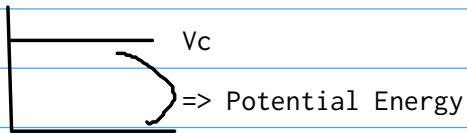原理: electric inductance
charging => discharging



C: Capacitance 電容量
charge amount 電荷量


$$Q_c = \int_0^{\tau} i_c(t) d\tau \quad // \quad C \text{ for charge amount}$$

$$V_c(t) = \frac{1}{C} \int_0^{\tau} i_c(t) d\tau$$

$$i_c(t) = C \frac{dV_c(\tau)}{d\tau}$$

$$C = \gamma AW$$

Inductor 電感線圈
- inductance

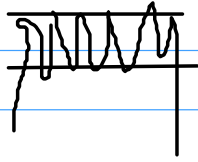

$$V(t) = L \frac{di(t)}{dt}$$

$$i(t) = \frac{1}{L} \int_0^t v(\tau) d\tau$$

L = 電感值

原理: electromagnetic inductance 電磁感應

電容跟電感連在一起 => 電磁學上的鐘擺模型

init: 電容充好電 (獲得電位能)

電容放電
電感產生抵制的感應電流
電容充電

力學能守恆的機械模型在電磁學上的等價

Capacitor 儲存電能
Inductor 調節能量
Resistor 損耗

How to solve an Electirc Circuit


- Find all the voltage and current values in that circuit
- All solution
 - voltage @ each vertex
 - current @ each edge (find loop currents) # for all loop in circuits
- Partial solution
 - input => |circuit| => output
- using Kirchhoff's Voltage & Current Laws

正負很重要!!!

KVL

- 其實就是能量守恆 (the conservation of potential energy)

T-circuit

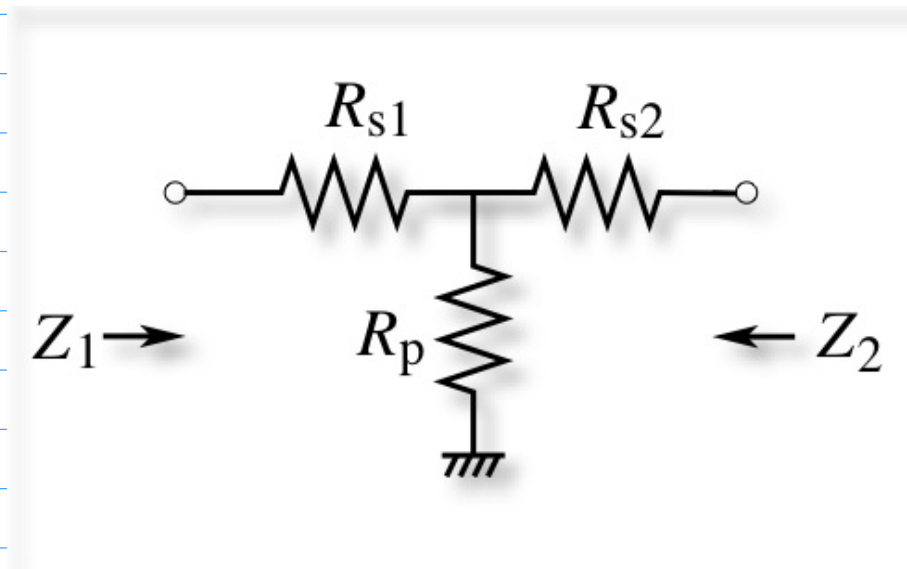

loop: 走完一圈的 edge

一定要新的 loop 找新的 vertex 多走, 沒有走過的 edge

KVL:

sum of all V_l in loop for all Loop is 0

$$\sum_{l \in \text{Loop}} V_l = 0$$

10/4


大助教：呂家哲 勿勿

Kirchhoff's Voltage and Current Laws (KCL & KVL)

- Basic Principles
- Basic Rules
- Simplification

Ex.

Ladder circuit (梯形電路)

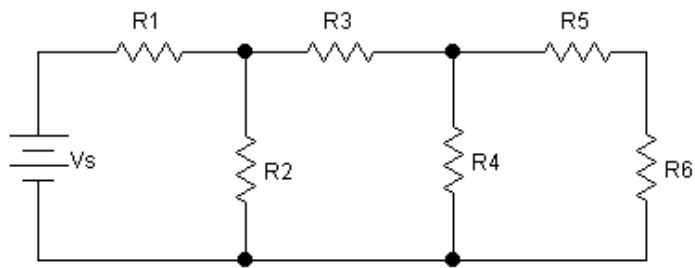

Vs Voltage source

R6 Load resistor

串聯 Serial connection

$$R1 + R2$$

同流分壓

$$VR = VR1 + VR2$$

$$iR = iR1 = iR2$$

$$R = R1 + R2$$

並聯 Parallel connection

$$R1 || R2$$

同流分壓

$$VR = VR1 = VR2$$

$$iR = iR1 + iR2$$

$$1/R = 1/R1 + 1/R2$$

$$R = R1R2 / (R1+R2)$$


Relation between Voltage of Nodes

KVL

- find loops => will solve loop currents
- the algebraic sum of voltage difference between the nodes in a solved loop of a circuit should always be zero


- Basic Principle

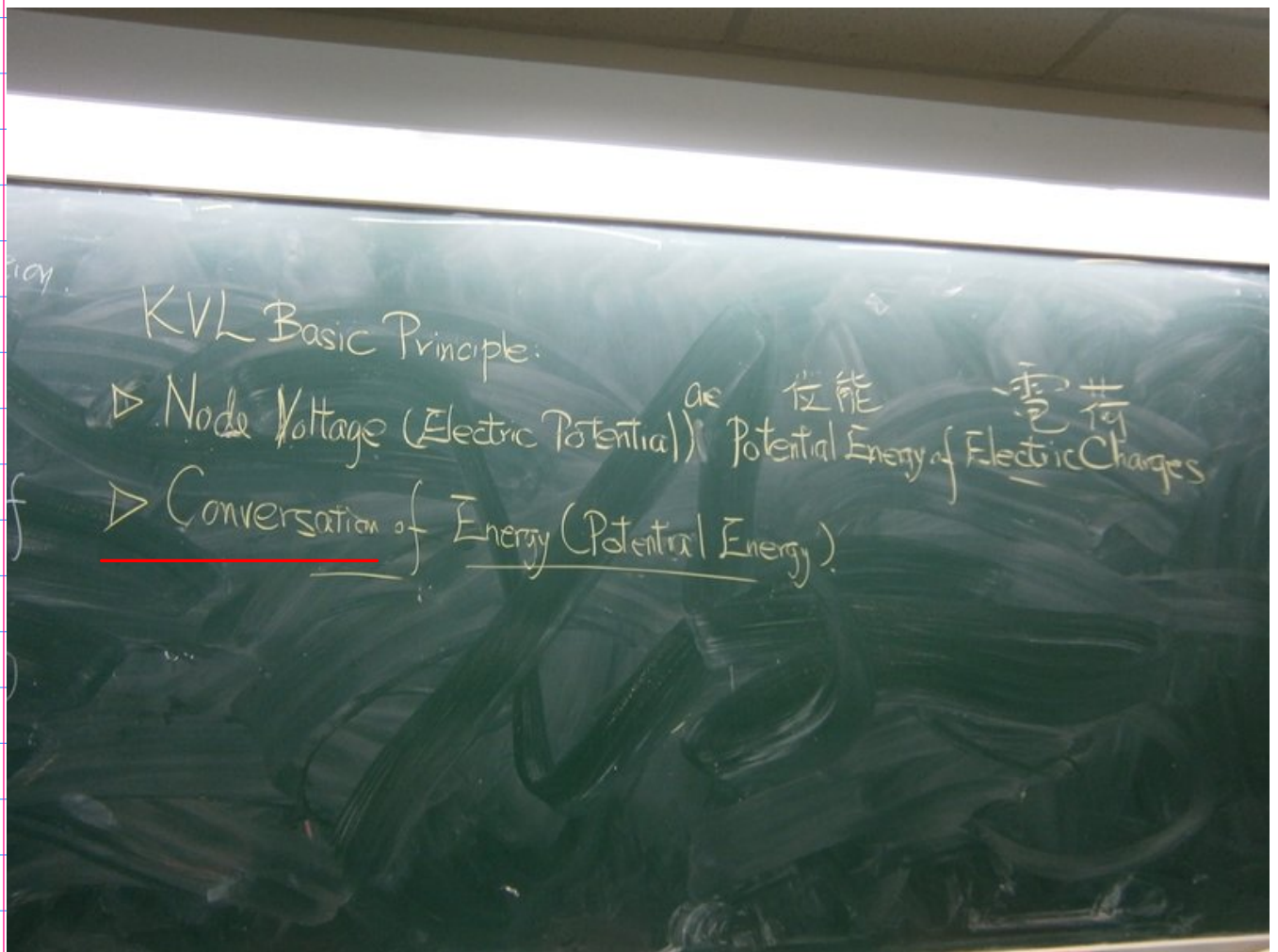- Node Voltage are Potential Energy of Electric charges
- Conservation of Energy (Electrical Potential)



能量的對話（誤

放個小趴照片 >////<

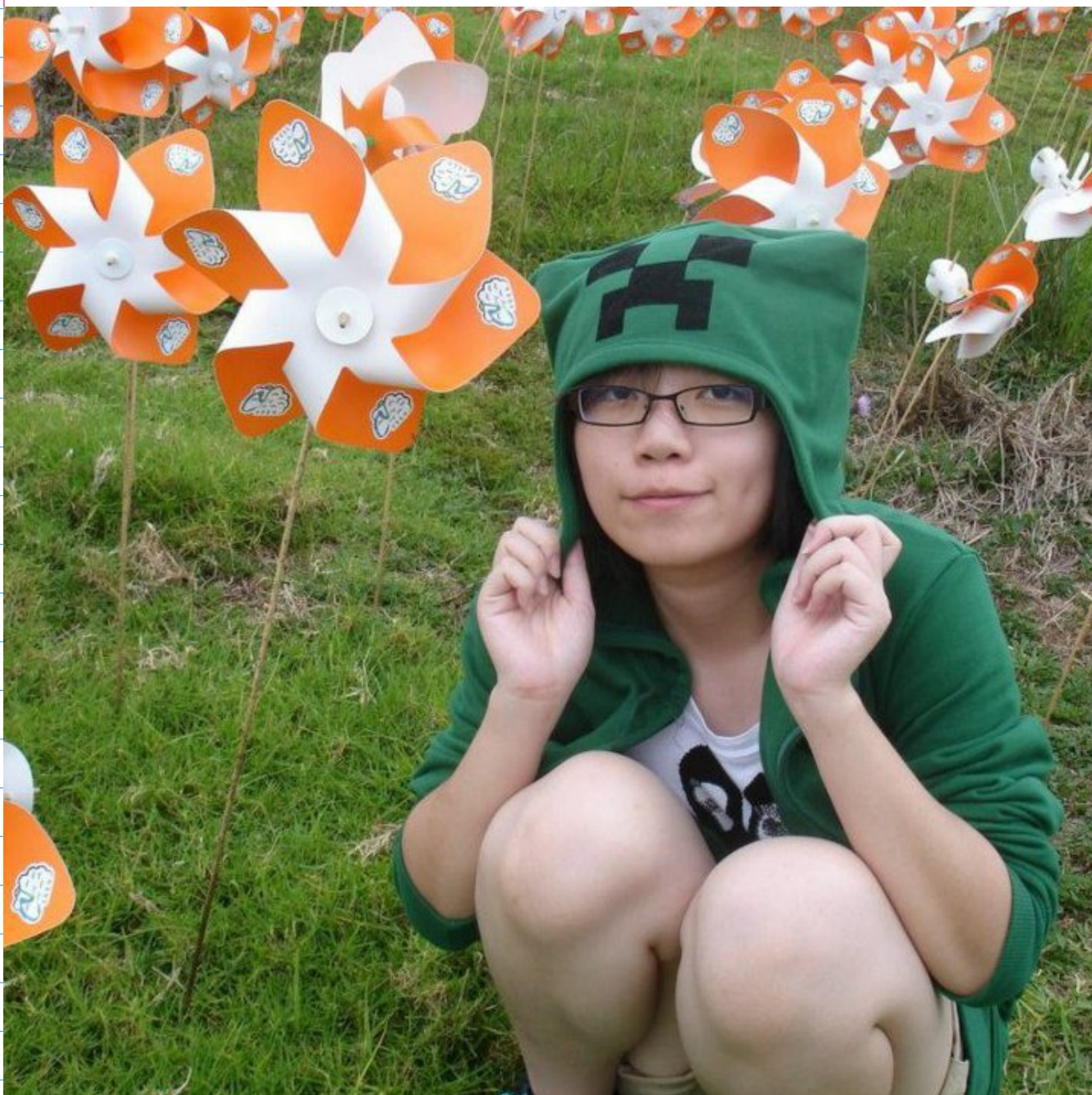



10/9

Rules for writing organized and correct circuit equations

KVL :

- For every closed loop (l), in an electric circuit the algebraic sum of voltage difference in the loop shall always be zero

loop:

- a path from one node back to itself without traversing any edge than once.

KVL use rules:

- identify all nodes in the circuit, start with the Ground node, other end of every component is a distinct node repeat the procedure until ALL components (edges) have been visited, AND ALL Nodes have been marked
- identify all loops in the circuit. Start from with Ground Node OR Upper Left Node. Identify a loop by traversing components connected to previous nodes in clockwise direction until you go back to the original node. Identify another new loop by including at least one new component again in clockwise direction until no new components can be included.
- Identify voltage difference across each components. Assign polarity (極性) which end node is position start from UPPER LEFT node which is likely to be the node with the Highest potential.

尋找方向: [左上 => 右下]

- Name the voltage difference using nodes or components.
E.g. V_{AB}
- write current Equations using KVL.
One equation from each loop along the loop current direction.

KCL:


- for each node N in a circuit, the algebraic sum of all currents flowing into and out of this node shall always be zero.

$$\sum_{K \in N} i_{NK} = 0$$

Underlying Principle:

- conservation of electric charges
- No charge shall be generated or destroyed in a circuit node

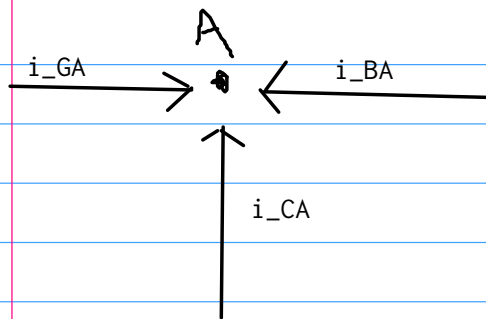- identify all nodes, using the same Rules as KVL
- assign every node with a distinct Node voltage
- one equation for every node



$$i_{GA} + i_{CA} + i_{BA} = 0$$

$$i_I + \frac{V_C - V_A}{R_1} + \frac{V_B - V_A}{R_2}$$

solve the Equation

10/11

Equivalent Circuits

Thevenin Equivalent
Norton Equivalent

求解：


voltage across and current pass through a pair of circuit nodes

circuit port:

a pair of distinct circuit nodes

solve voltage and current of that port (\Rightarrow one port) node

Thevenin Equivalent circuit

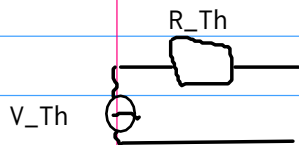

Equivalent voltage source

\Rightarrow Equivalent Resistance / Impedance

把複雜電路包裝成內部的獨立電壓源 V_{Th} 和與其串聯的等效電阻 R_{Th}

(從外部看的話是抽象的黑盒子)

For any linear circuits, the electric characteristics (v-i) of a specific point (a pair of distinct nodes) can always be modeled as an ideal voltage source V_{Th} and a serially connected passive element

Load Resistance


open circuits (斷路)

- resistance \Rightarrow infinity.
- $i = 0$ (no current pass through)

short circuits (短路)

- resistance \Rightarrow -
- $v = 0$ (no voltage difference between two terminals)
(M and N are not distinguishable nodes \Rightarrow merge into one node)

Principles:

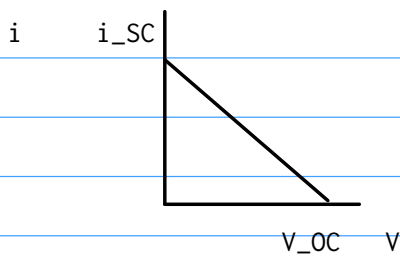

v-i characteristic \Rightarrow 線性組合

v_{OC}

- open circuit voltage
- $V_{NN} | i_{MN} = 0$ (V_{NN} @ $i_{MN} = 0$)

i_{SC}

- short circuit current
- $i_{SC} | V_{MN} = 0$

$$R_{Th} = V_{OV} / i_{SC}$$


線性 model: 只需要測量兩種極端情況 \Rightarrow 潮爽勿直接得到簡化後的電路特性

10/16

Thevenin & Norton Equivalent circuits for linear circuits Principles and applications

Thevenin & Norton Equivalent circuits principle

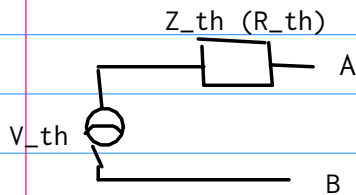- Linear circuits obey law of superposition
- Serially connected Linear Passive Elements



Voltage source

$V_{Th} = V_{AB}$ = open circuit voltage

i_{SC} = short circuit current

impedance : Z_{th}


Resistance: $R_{th} = v_{OC} / i_{SC}$

The voltage-and-current (v-i) characteristics of a port of any linear electric circuit can always be modeled as an equivalent source (V_{th}) connected in series with a linear passive element with impedance (Z_{th}) or resistance (R_{th})

The Dual Model (Norton):

Norton Equivalent circuit

Parallel connected passive elements

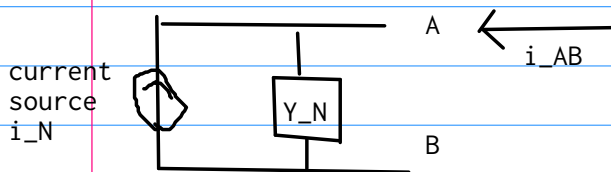

Admittance T_N

conductance (電導) $G_N : i / v = 1 / R_{Th}$




The voltage and current characteristics of port of any linear electric circuit can always be modeled as an equivalent source (i_N) connected in Parallel with a linear passive element with admittance (Y_N) or Conductance (G_N)

Rational (WHY?)

linear circuit, port

short circuit of a port when voltage across the two circuit nodes becomes ZERO
 $v_{AB} = 0$, $R_L = 0$

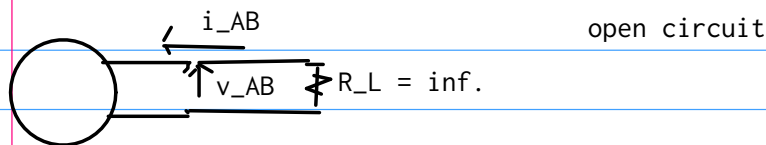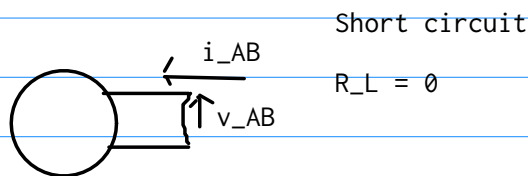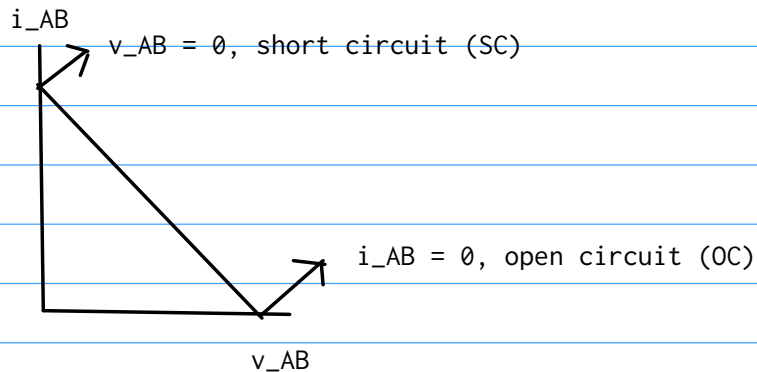open circuit of a port when current through the two circuit nodes becomes ZERO
 $i_{AB} = 0$, $R_L = \text{infinity}$.



$$KVL: (R : R_L)$$

$$-V_{Th} + V_R + V_{AB} = 0$$

$$V_{AB} = 0$$

$$-V_{Th} + V_R + V_{AB} = 0$$

$$V_R = V_{Th} \Rightarrow R_{Th} i_{OC} = V_{OC}$$

$$\Rightarrow R_{Th} = \frac{V_{OC}}{i_{SC}}$$

Ideal Voltage Source

- No internal (energy) loss
- No internal impedance / resistance ($R_{th} = 0$)

Ideal Current Source

- No internal (energy) loss
- No internal admittance / conductance ($G_N = 0$)

