

電子與電路學

-電路(Electric Circuit)+電子元件+電子線路(Electronic Circuit)

<DEF> Electric Circuit

A GRAPH - a collection of Vertices(端點) and Edges(連接)

whereby every edge contains exactly one electric component

and, every vertex has a specific electric potent where one of them is defined as 0 volt, i.e. Ground

-measurement

-Vertex → Electric Potential(V)(電壓): Potential Energy(位能)

-Edges → Current(I)(電流)

-Electric Power(P)(電力): $P = IV$

-能量以光速前進而非電子

<DEF> Ohm's Law

$$-R = \frac{V}{I} = \rho \frac{L}{A}$$

-R (resistor), ρ (resistivity)(電阻率), L(電阻長度), A(電阻截面積)

$$-E = \frac{V}{L} = \rho \frac{I}{A} = \rho J$$

-E(electric field strength), J(current density)

-宏觀(macroscopic)(電磁波長 $\lambda \gg$ 系統大小): $R=V/I$

-微觀(microscopic)(電磁波長 $\lambda \ll$ 系統大小): $E=\rho J$

<Syntax>

$v(t) / i(t)$: small → time varying value

V / I : capital → average of $v(t)/i(t)$

v_A / i_A : capital → reference with 0V/0A

v_a / i_a : small → reference with $V_A/I_A \rightarrow (v_a(t)-V_A)/(i_a(t)-I_A)$

<DEF> Root Mean Square

$$\widetilde{V}_A = V_A^{(rms)} = \sqrt{\frac{1}{T} \int_{t_0}^{t_0+T} V_A^2(t) dt}$$

$$P_T(t) = \frac{1}{T} \int_{t_0}^{t_0+T} i(\tau) v(\tau) d\tau = \frac{1}{T} \int_{t_0}^{t_0+T} \frac{v(\tau)}{R} v(\tau) d\tau = \frac{1}{T} \int_{t_0}^{t_0+T} \frac{v^2(\tau)}{R} d\tau$$

$$P_T(t) \propto \frac{1}{T} \int v^2(\tau) d\tau \propto v^{(rms)^2}$$

-Basic Electric Component







-Active Component

-Passive Component

<DEF> Active Component

Producer/Generator of signal power(訊號能量)


-Signal type

	Voltage	Current	
independent	  +/-: DC ~: AC		Signal Characteristic do not depend on other electric measurment in circuit
dependent	  +/-: DC ~: AC		----- [depend component]

<DEF> Passive Component

Consume signal power

-Resistor(R)(電阻): 能量耗損

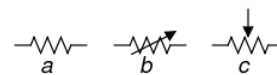


-v-i characteristic: Ohm's Law $\rightarrow R = \frac{V_R}{I_R}$

-Thermal effect(熱效應): Resistors produce heat when operating

-Thermal run away

-connection:

-Serial(串聯): $R_i + R_j$

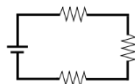


$$R_{total} = \sum_{i \in Serial} R_i$$

$$i_i = i_j \text{ where } i, j \in Serial$$

$$V_{total} = \sum_{i \in Serial} v_i$$

-Parallel(並聯): $R_i // R_j$

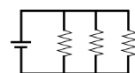


$$\frac{1}{R} = \sum_{i \in Parallel} \frac{1}{R_i}$$

$$v_i = v_j \text{ where } i, j \in Parallel$$

$$I_{total} = \sum_{i \in Parallel} i_i$$

-Capacitor(C)(電容): 位能保持與產生

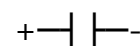

-Electric storage: charge(充電)/discharge(放電)

-Insulator(絕緣) medium/Air

-v-i characteristic:

$$Q_c = C v_c(t) = \int_0^t i_c(\tau) d\tau \rightarrow v_c(t) = \frac{1}{C} \int_0^t i_c(\tau) d\tau \rightarrow i_c(t) = C \frac{dv_c(t)}{dt}$$

-C(Capacitance)(電容量), Q(電量)

-Inductance(L)(電感)(線圈): 動能保持與產生

-Electro-magnetic inductance(電磁感應)

-電介質/Air

-v-i characteristic:

$$i_L(t) = \frac{1}{L} \int_0^t v_L(\tau) d\tau \rightarrow v_L(t) = L \frac{di_L(t)}{dt}$$

-L(電感值)

-Dual relation of v-i characteristic: Capacitor \leftrightarrow Inductance

<CONCEPT> Linearity

Law of Superposition(疊加原理): 訊號可以由不同訊號源經疊加產生

$$S(ax_1 + bx_2) = aS(x_1) + bS(x_2)$$

<How to SOLVE an Electric Circuit>

-Complete/Full solution: find ALL the voltage (at each vertex) and current (through each edge) values in the circuit

-Partial Solution: find the voltage and current values at Input Node and Output Node

<DEF> Kirchhoff's Voltage & Current Law (KVL & KCL)

-KVL: Algebraic sum of all Voltage differences between the nodes in a Closed Loop of a circuit should always be ZERO

-closed loop: a path from one node back to itself without traversing any edge more than once

-node voltage as potential energy of electric charges

-Conservation of Energy(能量守恆定律)

$$\sum_{i \in \text{Closed-Loop}} v_i = 0$$

-(+v): same direction as flow voltage

(- v): opposite direction to flow voltage

-Use Rule:

-Identify all Nodes in the circuit

-start with GROUND Node

-other end of every component is a distinct node

-repeat the procedure until all components have been visited and all nodes have been marked

-assign every node (except Ground) with a distinct node voltage

-Identify all Loops in the circuit

-start with GROUND Node (or Upper-Left Node)

-identify a loop by traversing components connected to the previous node until going back to the original node (in clockwise direction)

-identify another new loop by including at least one new component until no new component can be included

- Identify voltage difference across each component
 - assign Polarity(極性) which end node is positive
 - start from Upper-Left Node which is likely to be the node with highest potential
 - name the voltage differences using end nodes or components

$$-V_{(+node)(-node)} \text{ Or } V_{(component)}$$

- write Circuit Equations using KVL

- one equation for every loop along loop circuit direction

-KCL: Algebraic sum of all Currents flow into (+ve) and out of (-ve) a node in a circuit should always be ZERO

- no electric charges shall be generated or destroyed in a circuit node
- Conservation of electric charges

$$\sum_{i \in \text{Node}} i_i = 0$$

- Use Rule:

- Identify all Nodes in the circuit
- Identify voltage difference across each component
- write Circuit Equations using KCL
- one equation for every node

<DEF> Open Circuit & Short Circuit

-Open Circuit(O.C. 斷路)

- NULL Condition: $i_{AB} \equiv 0 \rightarrow R \rightarrow \infty$

-Short Circuit(S.C. 短路)

- NULL Condition: $v_{AB} \equiv 0 \rightarrow R = 0$

- A and B are NOT distinguishable nodes \rightarrow merge into one node

<CONCEPT> Equivalent Circuit(等效線路)

Simplify the process of solving EE (Linear) circuit

-Circuit Port: a Pair of distinct circuit nodes

-One Port Circuit



- Thevinin Equivalent Circuit: for any linear circuit, the electric characteristic (v-i characteristic) of a specific port can always be modeled as an Ideal Voltage Source (v_{th}) and a SERIALY connected passive element with Impedance(阻抗) (Z_{th}) or Resistor (R_{th})

$$v_{oc} \triangleq v_{AB}|_{i_{AB}=0}; v_{oc}(\text{open circuit voltage})$$

$$i_{sc} \triangleq i_{AB}|_{v_{AB}=0}; i_{sc}(\text{short circuit voltage})$$

$$v_{th} = v_{oc}$$

$$R_{th} = \frac{v_{oc}}{i_{sc}}$$

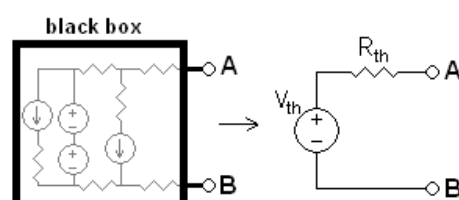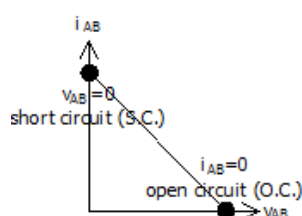

-short circuit: $v_{AB}=0 \rightarrow R=0$; open circuit: $i_{AB}=0 \rightarrow R \rightarrow \infty$

KVL: (open circuit) $v_{th}-v_R(=0)-v_{AB}(=v_{oc})=0 \rightarrow v_{th}-v_{oc}=0 \rightarrow v_{th}=v_{oc}$

(short circuit) $v_{th}-v_R-v_{AB}(=0)=0 \rightarrow v_{th}=v_{oc}=v_R=R_{th}i_{sc} \rightarrow R_{th}=v_{oc}/i_{sc}$

-really practical way

-calculate v_{th} : using Voltage Divider Formula

-calculate R_{th} : estimate internal impedance

-turn off all internal signal source


-ideal voltage source \rightarrow short circuit

-ideal current source \rightarrow open circuit

-Norton Equivalent Circuit: for any linear circuit, the electric characteristic (v-i characteristic) of a specific port can always be modeled as an Ideal Current Source (i_{no}) and a PARALLEL connected passive element with Admittance (Y_{no}) or Conductance(電導) (G_{no})

$$i_{no} = i_{sc}$$
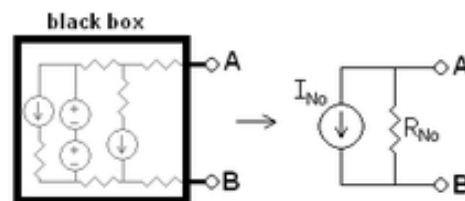
$$G_{no} = \frac{i_{sc}}{v_{oc}} = \frac{1}{R_{th}}$$



<CONCEPT> Ideal Voltage/Current Source

-Ideal Voltage Source

-No internal loss

-No internal impedance/resistor $\rightarrow R_{th}=0$

-Ideal Current Source

-No internal loss

-No internal admittance/conductance $\rightarrow G_{no}=0$

<DEF> Transfer Function

always quantities of input vs. output signal

Four possible combinations depending on choice of input/output quantities

(voltage/current)

Specify the voltage/current condition (O.C./S.C.) for measuring Transfer Function

-Voltage Ratio (Voltage Gain):

$$A_v \triangleq \frac{v_{out}}{v_{in}} \Big|_{i_{out}=0} ; \text{ (O. C.) } A(\text{amplification})$$

-Current Ratio (Current Gain)

$$A_i \triangleq \frac{i_{out}}{i_{in}} \Big|_{v_{out}=0} ; \text{ (S. C.) }$$

-Trans-Resistance

$$Z_T \triangleq \frac{v_{out}}{i_{in}} \big|_{i_{out}=0} ; (\text{O.C.})$$

-Trans-Conductance

$$Y_T \triangleq \frac{i_{out}}{v_{in}} \big|_{v_{out}=0} ; (\text{S.C.})$$

<CONCEPT> Coupling(耦合)

-according to the electric characteristic of input/output signal

-Voltage Coupling

-Thevinin Equiv.

$$v_s^1 = A_v v_{in}^1$$

$$v_s^1 = v_{R_{out}^1} + v_{R_{in}^2} = (R_{out}^1 + R_{in}^2) i$$

$$v_{in}^2 = R_{in}^2 i = \frac{R_{in}^2}{(R_{out}^1 + R_{in}^2)} v_s^1 \rightarrow \frac{v_{in}^2}{R_{in}^2} = \frac{v_s^1}{(R_{out}^1 + R_{in}^2)}$$

-Current Coupling

-Norton Equiv.

$$i_s^1 = A_i i_{in}^1$$

$$i_s^1 = i_{Y_{out}^1} + i_{Y_{in}^2} = (Y_{out}^1 + Y_{in}^2) v$$

$$i_{in}^2 = Y_{in}^2 v = \frac{Y_{in}^2}{(Y_{out}^1 + Y_{in}^2)} i_s^1 \rightarrow \frac{i_{in}^2}{Y_{in}^2} = \frac{i_s^1}{(Y_{out}^1 + Y_{in}^2)}$$

-according to the characteristic of transferred signal

-DC Coupling: including DC and AC component

-AC Coupling: including AC component only

-Coupling Capacitor(耦合電容) filter out the output DC components


-if DC signal

$$v_c(t) = v_{DC} (1 - e^{-t/\tau}) ; \tau = R_L C$$


$$i_c(t) = \frac{v_{DC}}{R_L} (e^{-t/\tau}) ; \tau = R_L C$$

$$\text{-KVL: } v_{DC} - v_C - v_L = 0 \rightarrow v_L = v_{DC} - v_C$$

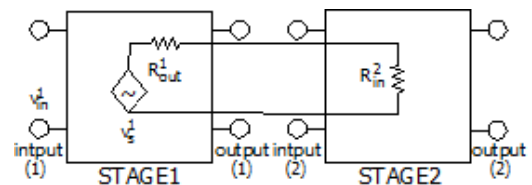
$$\text{when } t \rightarrow \infty \rightarrow v_C \rightarrow v_{DC} \rightarrow v_L \rightarrow 0$$




Voltage Coupling

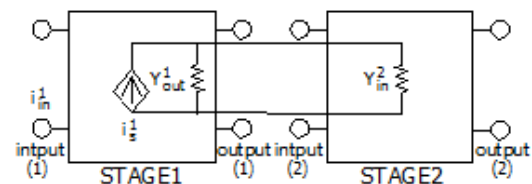

Current Coupling

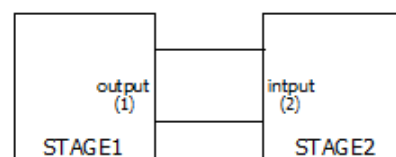

Direct Coupling (DC)

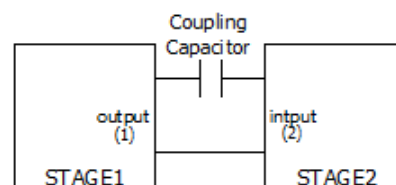

Indirect Coupling (AC)

