

1.1

Linear system:

Page 7 definition.1

(from Note EE Circuit - Basic & System Theory(Zao).pdf)

or

$$T\{X_1(t) + X_2(t)\} = T\{X_1(t)\} + T\{X_2(t)\} = y_1(t) + y_2(t)$$

$$T\{A \cdot X_1(t)\} = A \cdot y_1(t)$$

Superposition:

In any linear circuit containing multiple independent sources, the current or voltage at any point in the network may be calculated as the algebraic sum of the individual contributions of each source acting alone.

1.2

Open circuit, short circuit, parallel connections, serial connections:

Page 6, 5. electric circuit, operation

(from Note EE Circuit - Basic & System Theory(Zao).pdf)

1.3

Electric power $p(t)$, voltage $v(t)$, current $i(t)$:

Page 1, 公式.2 + 公式.4 推导出公式.6

(from Note EE Circuit - Basic & System Theory(Zao).pdf)

1.4

Root-mean-square voltage value, V_{rms} :

Page 2, 公式 9

(from Note EE Circuit - Basic & System Theory(Zao).pdf)

1.5 Kirchhoff's voltage and current (KVL/KCL):

Page 7, 6 circuit laws

(from Note EE Circuit - Basic & System Theory(Zao).pdf)


1.6 Thevenin and Norton equivalent circuits:

(a) Page 9, theorem 4 & 5

(b) superposition

2.1

2.1

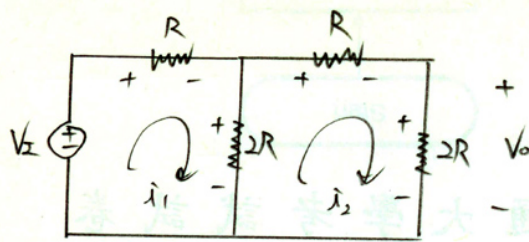

$$\begin{cases} V_I - Ri_1 - 2R(i_1 - i_2) = 0 \\ 2R(i_1 - i_2) - Ri_2 - 2Ri_2 = 0 \end{cases}$$

$$\Rightarrow \begin{cases} V_I - 3Ri_1 + 2Ri_2 = 0 \\ 2Ri_1 - 5Ri_2 = 0 \end{cases} \quad \begin{matrix} \leftarrow & \rightarrow \\ V_I - \frac{15}{2}Ri_2 + 2Ri_2 = 0 \end{matrix}$$

$$\rightarrow i_1 = \frac{5}{2}i_2$$

$$\therefore V_I = \frac{11}{2}Ri_2 \rightarrow i_2 = \frac{2}{11} \cdot \frac{V_I}{R}$$

$$\therefore V_O = \frac{2}{11} \times \frac{V_I}{R} \times 2R = \frac{4}{11} V_I$$


$$V_O = \frac{\frac{6}{5}R}{R + \frac{6}{5}R} \times \frac{2R}{2R + R} \times V_I = \frac{4}{11} V_I$$

2.2


2.2

① $V_{th} = \frac{4}{11} V_I$

② R_{th}
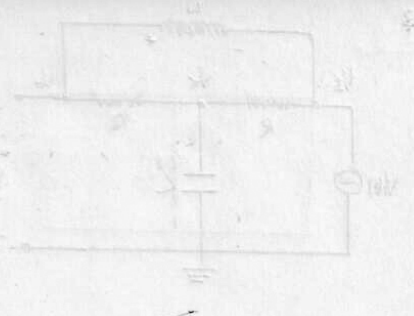
$$R_{th} = \left[(R // 2R) + R \right] // 2R = \frac{10}{11} R$$

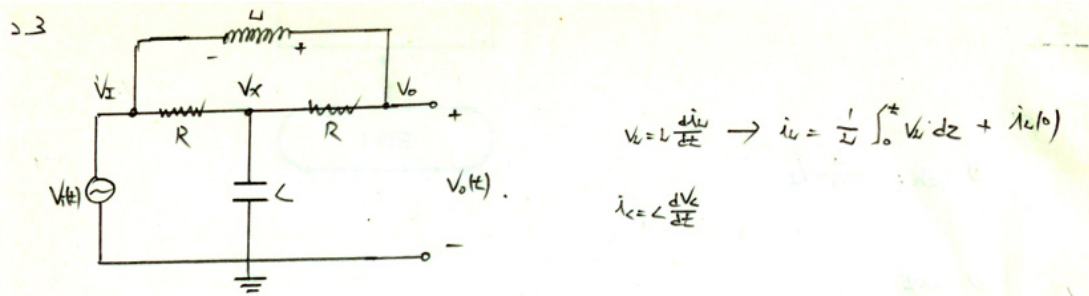
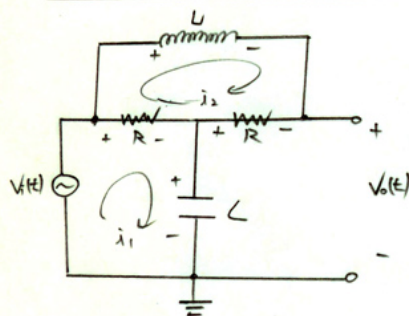
2.3



KVL:

for v_x : $\frac{v_x - v_i}{R} + C \frac{dv_x}{dt} + \frac{v_x - v_o}{R} = 0$

for v_o : $\frac{v_o - v_x}{R} + \frac{1}{L} \int_0^t (v_o - v_x) dz + i_L(0) = 0$



KVL:

for i_1 : $v_m - R(i_1 - i_2) - \left[\frac{1}{C} \int_0^t i_1 dz + v_C(0) \right] = 0$


for i_2 : $R(i_1 - i_2) + R(-i_2) - L \frac{di_2}{dt} = 0$

2.4

2.4 Wheatstone bridge.

(a) $V_0 = 0$.

KCL

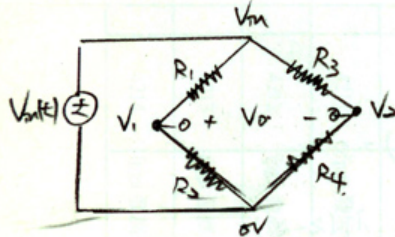

V_1, V_2 .

for V_1 : $\frac{V_1 - V_m}{R_1} + \frac{V_1}{R_2} = 0$ - (1)

for V_2 : $\frac{V_2 - V_m}{R_3} + \frac{V_2}{R_4} = 0$ - (2)

整理 (1)

$V_1 \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{V_m}{R_1}$

$V_1 = \frac{R_1 R_2}{R_1 + R_2} \times \frac{V_m}{R_1} = \frac{R_2}{R_1 + R_2} V_m$

整理 (2)


$V_2 = \frac{R_4}{R_3 + R_4} V_m$

$\therefore V_0 = V_1 - V_2 = 0$.

$\therefore \frac{R_2}{R_1 + R_2} = \frac{R_4}{R_3 + R_4}$

$\frac{1}{\frac{R_1}{R_2} + 1} = \frac{1}{\frac{R_3}{R_4} + 1}$

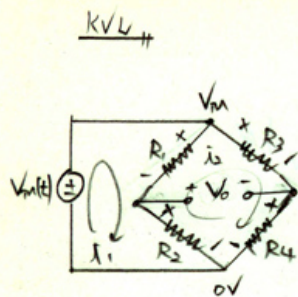$\therefore \frac{R_1}{R_2} = \frac{R_3}{R_4}$



假设 i_1, i_2

$$\begin{cases} i_1: V_m - R_1(i_1 - i_2) - R_2(i_1 - i_2) = 0 & \text{--- (1)} \\ i_2: R_2(i_1 - i_2) + R_1(i_1 - i_2) - R_3 i_2 - R_4 i_2 = 0 & \text{--- (2)} \end{cases}$$

from (1)

$$V_m - (R_1 + R_2)(i_1 - i_2) = 0$$

$$V_m + i_2(R_1 + R_2) = i_1(R_1 + R_2)$$

$$\therefore i_1 = \frac{V_m}{R_1 + R_2} + i_2 \quad \text{--- (3)}$$

整理 (2)

$$(R_1 + R_2)(i_1 - i_2) - (R_3 + R_4)i_2 = 0$$

$$(R_1 + R_2)i_1 - (R_1 + R_2 + R_3 + R_4)i_2 = 0$$

(3) 代入 (2)

$$V_m + (R_1 + R_2)i_2 - (R_1 + R_2 + R_3 + R_4)i_2 = 0$$

$$\therefore V_m - (R_3 + R_4)i_2 = 0$$

$$i_2 = \frac{V_m}{R_3 + R_4} \quad \text{--- (4)}$$

(4) 代入 (3)

$$i_1 = \frac{V_m}{R_1 + R_2} + \frac{V_m}{R_3 + R_4} \quad \text{--- (5)}$$

$$\therefore V_0 = [V_m - R_1(i_1 - i_2)] - [V_m - R_3 i_2] = 0$$

$$\Rightarrow \cancel{V_m} \left(1 - \frac{R_1}{R_1 + R_2}\right) = \cancel{V_m} \left(1 - \frac{R_3}{R_3 + R_4}\right)$$

$$\frac{R_2}{R_1 + R_2} = \frac{R_4}{R_3 + R_4} \Rightarrow \frac{R_1}{R_2} = \frac{R_3}{R_4}$$

2.4

(b)

$$\left\{ \begin{array}{l} R_1 = R_3 = R \\ V_0 = V_1 - V_2 = \frac{1}{2} V_2 \end{array} \right.$$

$$\left\{ \begin{array}{l} V_1 = \frac{R_2}{R_1 + R_2} V_2 \\ V_2 = \frac{R_4}{R_3 + R_4} V_1 \end{array} \right.$$

$$\therefore V_0 = \left(\frac{R_2}{R_1 + R_2} - \frac{R_4}{R_3 + R_4} \right) V_2 = \frac{V_2}{2}$$

$$= \frac{R_2(R_3 + R_4) - R_4(R_1 + R_2)}{(R_1 + R_2)(R_3 + R_4)} = \frac{1}{2}$$

$$= \frac{R_2(R + R_4) - R_4(R + R_2)}{(R + R_2)(R + R_4)} = \frac{1}{2}$$

$$= \frac{RR_2 + \cancel{R_2R_4} - \cancel{RR_4} - R_2R_4}{R^2 + RR_2 + RR_4 + R_2R_4} = \frac{1}{2}$$

$$= \frac{RR_2 - RR_4}{R^2 + RR_2 + RR_4 + R_2R_4} = \frac{1}{2}$$

$$2RR_2 - 2RR_4 = R^2 + RR_2 + RR_4 + R_2R_4$$


$$RR_2 = R^2 + 3RR_4 + R_2R_4$$

$$R(R_2 - R) = R_4(3R + R_2)$$


$$R_4 = \frac{R(R_2 - R)}{-(R_2 + 3R)}$$

$$R_2 > R \quad \# \quad \text{解法正确}$$


2.5

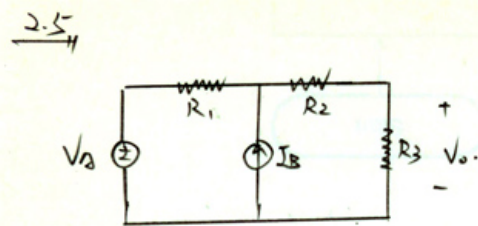

for V_0 :

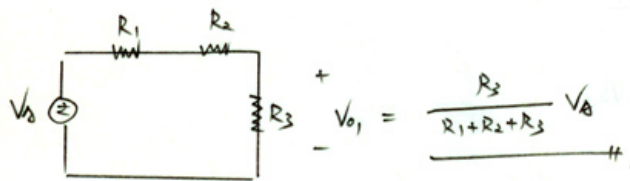

for I_B :

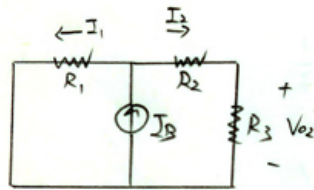

$$\begin{cases} R_1 I_1 = I_2 (R_2 + R_3) \\ I_1 + I_2 = I_B \end{cases}$$

$$\rightarrow I_1 = I_B - I_2$$

$$R_1 (I_B - I_2) = I_2 (R_2 + R_3)$$

$$R_1 I_B - R_1 I_2 = I_2 (R_2 + R_3)$$

$$\therefore I_2 = \frac{R_1 I_B}{R_1 + R_2 + R_3}$$

$$\therefore V_{02} = I_2 R_3 = \frac{R_1 R_3}{R_1 + R_2 + R_3} I_B$$

$$\therefore V_0 = V_{01} + V_{02}$$

$$= \frac{R_3}{R_1 + R_2 + R_3} V_0 + \frac{R_1 R_3}{R_1 + R_2 + R_3} I_B$$