

Operational Amplifier (OP, OpAmp)


Ideal Characteristic

(i) Basic Building Block of
most analog circuit.

(ii) function as Ideal

(differential) voltage amplifier

Voltage input output (single Ended)

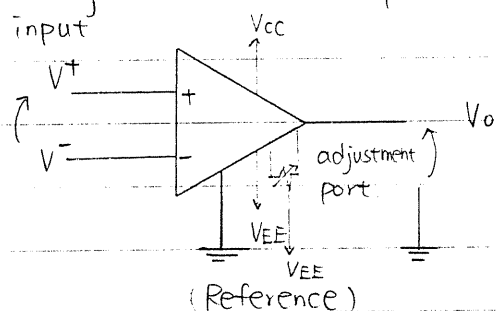

$$V_{diff} = V^+ - V^-$$

$$V_{EE} < V_o < V_{CC}$$


(+0.2V) (-0.2V)

Output voltage swing

$$V_{EE} + 0.2 < V_o < V_{CC} - 0.2$$

Adjustment port:

DC offset Calibration

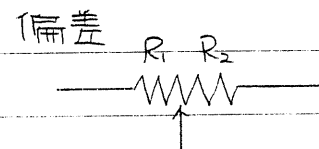

Without calibration

$$V_o(\text{actual}) \neq 0V$$

Ideal Voltage Amplifier

(i) infinite input impedance (Z_{in})

$$Z_{in} = \frac{V_{diff}}{I_{diff}} \rightarrow \infty \quad 1M\Omega \sim 10M\Omega$$

$$\Rightarrow i^+, i^- \text{ input current} \\ \simeq 10^{-6} A \text{ (nA)}$$

(ii) Zero output impedance

$$Z_{out} = \frac{V_o}{I_o} \simeq 0 \quad 10\Omega$$

output is an ideal voltage source

(iii) Infinite open-loop Voltage gain

$$A_{vo} = \frac{V_o}{V_{diff}} \rightarrow \infty \quad 10^5 \sim 10^7$$

$$\Rightarrow V_{diff} \rightarrow 0 \quad V^+ \simeq V^-$$

$$|V_o|_{max} \simeq 10V \Rightarrow |V_{diff}|_{max} \simeq 10^{-5} \sim 10^{-7} V$$


$$(A_{vo})_{db} = 20 \log_{10} A_{vo}$$

$$10^5 \sim 10^7 \Rightarrow 100 \sim 140 \text{ db}$$



Virtual Node

single input node: 不吸收電流

$$\therefore i^+, i^- \simeq 0$$

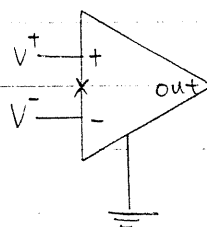

OpAmp Inverting Voltage Amplifier

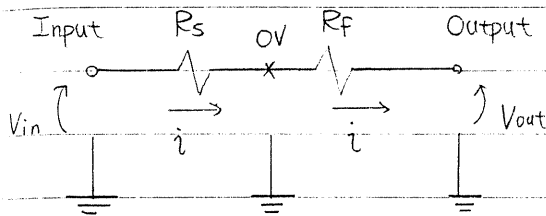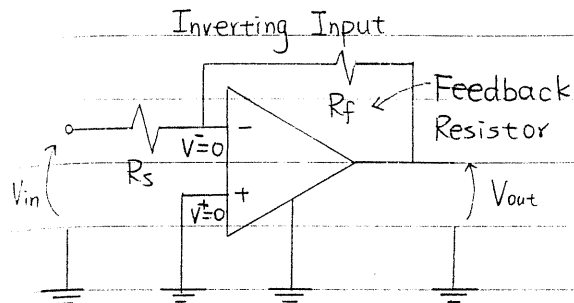


$$\frac{V_{in} - 0}{R_s} = \frac{0 - V_{out}}{R_f} \Rightarrow \frac{V_{out}}{V_{in}} = -\frac{R_f}{R_s}$$

$$R_{in} (\text{input impedance}) = R_s$$

$$R_{out} (\text{output impedance}) = R_f$$


Non Inverting voltage Amplifier

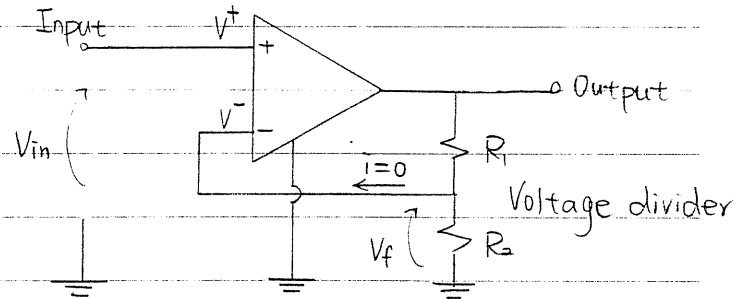

$$V_f(t) = \left(\frac{R_2}{R_1 + R_2} \right) V_{out}$$


feedback voltage

$$V_{in}(t) = V_f(t)$$

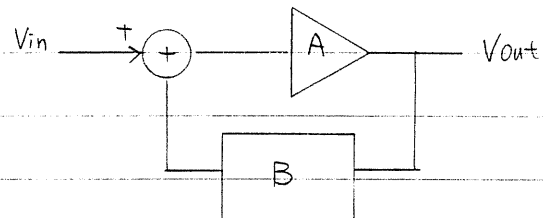

$$\frac{V_{out}}{V_{in}} = B^{-1} \quad f A \rightarrow \infty$$

Inverting Adder

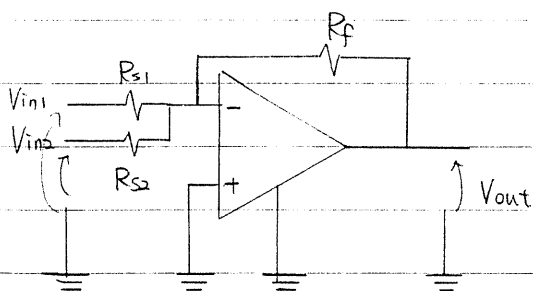

$$V_{out} = -\frac{R_f}{R_{s1}} V_{in1} - \frac{R_f}{R_{s2}} V_{in2}$$