

National Chiao Tung University
Computer Science Department

INTRODUCTION TO ELECTRIC AND ELECTRONIC CIRCUITS

Assignment [1] : Circuit Models and Coupling

Instructor:	Prof. John K. Zao
Issuing date:	Tuesday, November 27, 2012
Submission due date:	Tuesday, December 11, 2012

Homework Reading


- | | |
|---|--|
| ❖ Zao & Peng, “EE Circuit Notes”, 2008. | pp. 7 – 15 |
| ❖ Strum & Ward, “Electric Circuits and Networks”, 1985. | Ch. 2, pp. 38 – 48;
Ch. 10, pp. 338 - 384 |

Part 1. Conceptual Questions

- 1.1 Please define the following *characteristic parameters* of two-port electrical circuits.
- | | |
|--|------|
| ➤ <i>Input Impedance under no load condition</i> | 2% |
| ➤ <i>Output Impedance with respect to voltage and current inputs</i> | 2×2% |
| ➤ <i>Voltage Gain</i> | 2% |
| ➤ <i>Current Gain</i> | 2% |
- Please specify the *necessary voltage/current conditions* at the output in order to measure current and voltage gains properly. Please give the reason why. 4%
- 1.2 Please describe the ways to determine *output impedance* of a linear electrical circuit based on the *law of reciprocity*. 4%
- 1.3 Please define *DC* and *AC voltage coupling* between two circuits. Why AC coupling is also known as *capacitive coupling*? 6%
- 1.4 Please define *voltage* and *current coupling* between two circuits. 4%
- Please explain the concept of *perfect coupling*. 2%
- What are the necessary conditions of *perfect voltage* and *current coupling* in terms of *input/output impedances* of the coupled circuits? 2×4%
- Where are the implications of *perfect voltage/current coupling* towards the design of *ideal voltage or current amplifiers*? 2×2%

Part 2. Analytical Questions

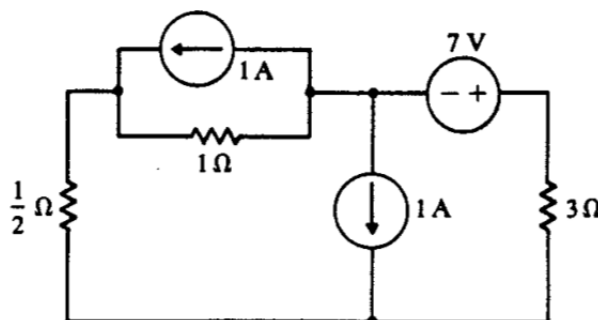- 2.1 Given the linear electrical circuit on the next page, please use *KVL loop analysis* to determine the *current* through the 3Ω resistor. 10%




Then, use *KCL nodal analysis* to determine the *voltage* across the 0.5Ω resistor. 10%

2.2 In the following *RC circuit*, the voltages $v_1(t)$ and $v_2(t)$ at $t = t_0$ are given:

$$v_1(t_0) = +2V, \quad v_2(t_0) = +5V, \quad \left. \frac{dv_2}{dt} \right|_{t=t_0} = -10V/s$$

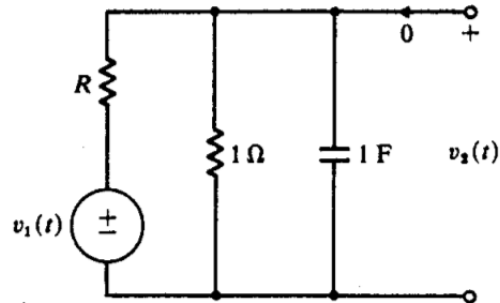Please determine the value of resistor R . 15%



2.3 Given the following Π -circuit, please determine the characteristics of this *two-port circuit*:

- Input impedance R_{in} with *no load* attached to v_o ; 6%
- Input impedance R_{in} with load R_L attached to v_o ; 2%
- Output impedance R_{out} observed across v_o ; 6%
- Thevenin equivalent of the entire circuit; 8%
- Voltage transfer function $A_v \stackrel{\text{def}}{=} v_o/v_i$ of the circuit. 4%

